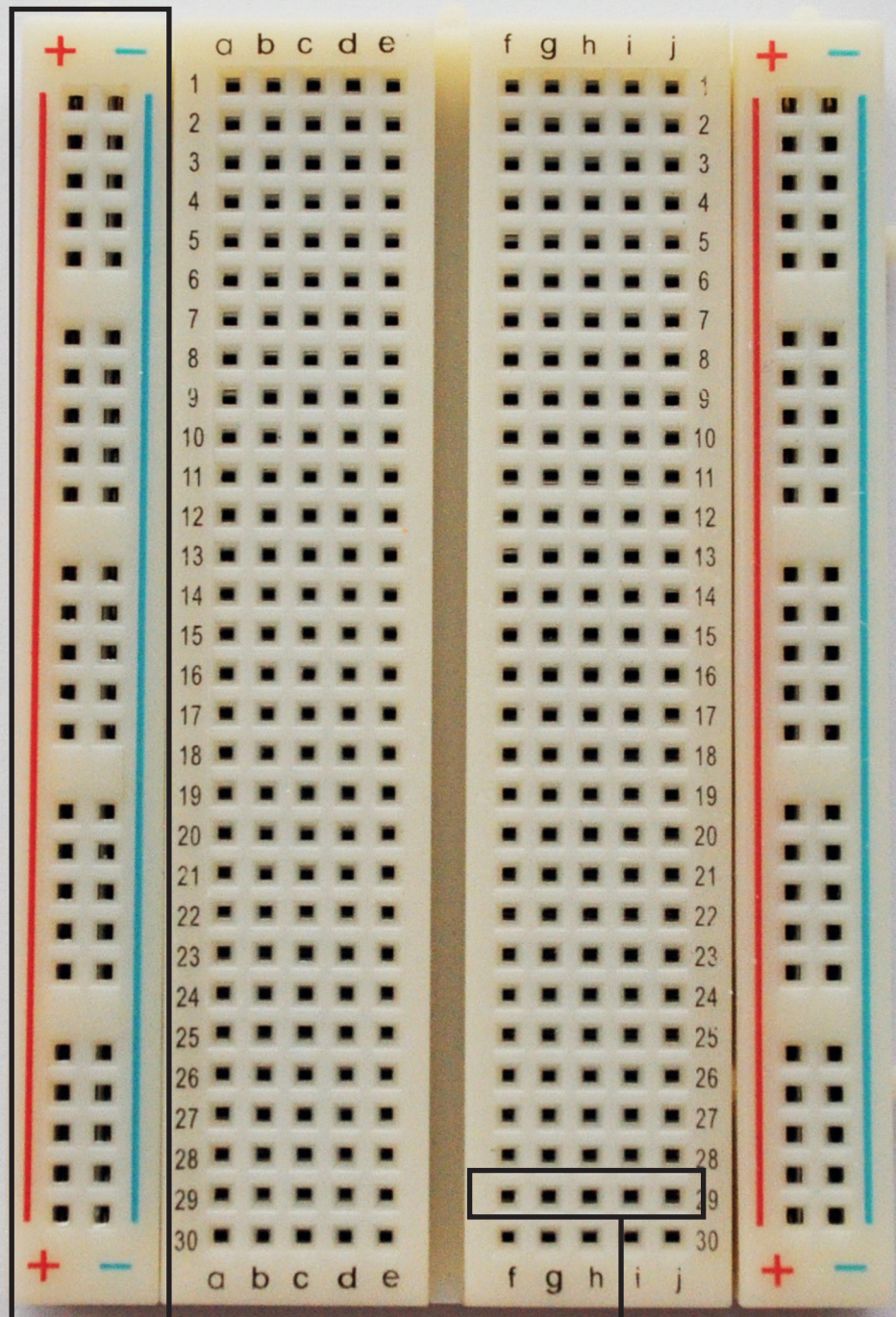


# fabschoolino Working with a breadboard

CODE / HACK / PLAY

Using a breadboard enables you to create an electrical circuit without having to solder, which means you can test a circuit quickly and easily.



The vertical lines are all connected to one another. The red line is the power supply while the blue line is for grounding.


The horizontal holes on each side of the breadboard are connected to each other. All the parts that you insert will be connected to each other in the row.



# fabschoolino Working with a breadboard


CODE / HACK / PLAY

1

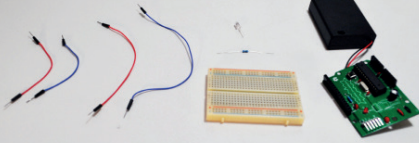


You will need:  
red wires (long and short),  
blue wires (long and short), a  
breadboard, 1K ohm resistor, an  
LED, and a Fabschoolino.

2

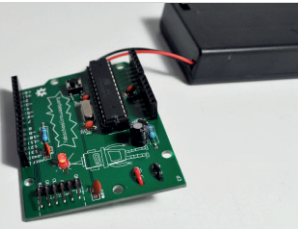


Turn on the Fabschoolino.  
Turn the switch on the battery  
from off to on. If everything is  
working, the LED will flash when  
you press the reset button.

3

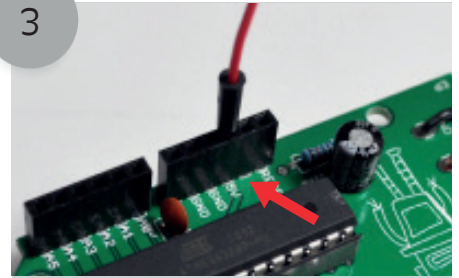


Insert the end of your long red  
wire in the header pin where 5V  
is written.

4

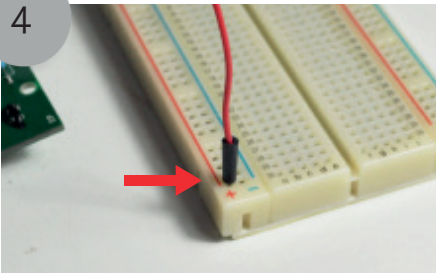


Now insert the other end of  
the long red wire into the  
breadboard on the side where  
you see the red plus sign.

5

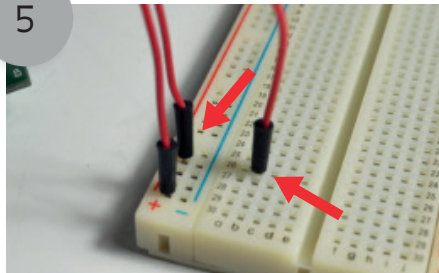


Take your short red wire and  
insert it (just like you did with  
the long wire) into the side with  
the red plus sign. Then plug  
the other end of the wire into a  
hole.

6

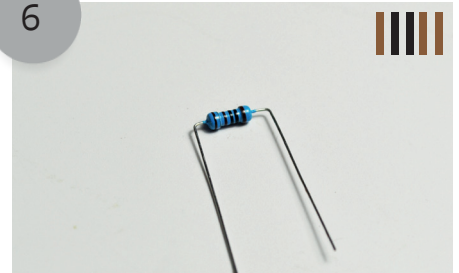


Take the 1K ohm resistor and  
bend its legs.

7

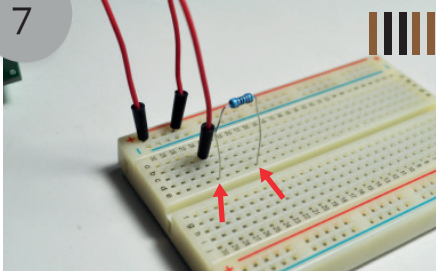


Insert one leg into the same  
row as your short wire. Insert  
the other leg in a different row  
further down as shown above.

8

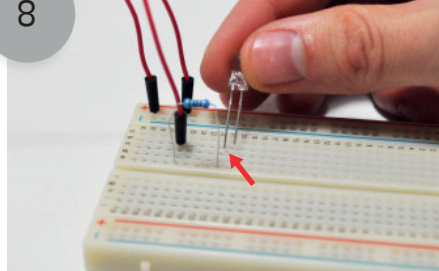

Now it's time to place your LED  
on the board. NOTE: The LED  
has both a long and a short leg.  
Make sure the long leg ends up  
in the same row as the resistor.

9

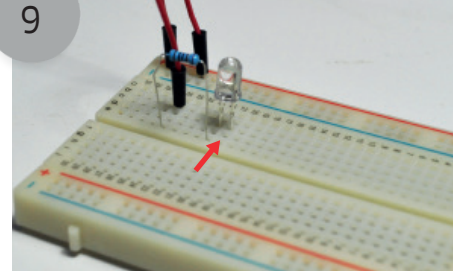

Your LED's short leg goes  
in a row further down the  
breadboard.




waag society

# fabschoolino Working with a breadboard


CODE / HACK / PLAY

10

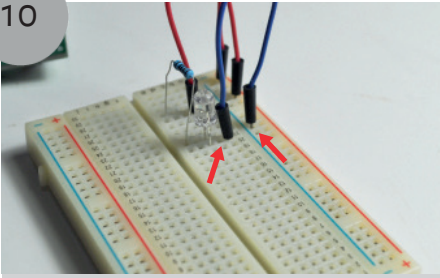

Place the short blue wire in the same row as the short leg of your LED. Insert the other end of the wire on the side where you see the blue minus sign.

11

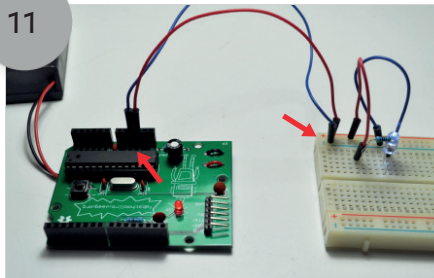

Place the long blue wire next to the long red wire on the side with the minus sign. Insert the other end of the wire into the Fabschoolino where GND is written. If everything works, you'll see your LED turn on.



waag society